

Part A – Course

Simple control circuits without limit switches

Exercise 1:	Sorting device Double-acting cylinder, directly actuated, manually	A-3
Exercise 2:	Component selection on conveyor belt Double-acting cylinder, directly actuated, manually	A-13
Exercise 3:	Lifting station Single-acting cylinder, directly actuated, manually	A-23
Exercise 4:	Bending device Double-acting cylinder, latching	A-29
Exercise 5:	Press-fitting device Double-acting cylinder, latching, return stroke using pressure switch	A-33
Exercise 6:	Stamping machine Double-acting cylinder, differential circuit	A-39
Exercise 7:	Door control Double-acting cylinder, interlock, INCHING operation	A-43

Control circuits with limit switches

Exercise 8:	Machining unit Differential circuit, return stroke using limit switch	A-49
Exercise 9:	Feed for drilling machine Rapid-traverse feed circuit, speeds controlled by limit switch	A-53
Exercise 10:	Press Pressure control circuit with limit switch and pressure switch	A-59
Exercise 11:	Feed device Pressureless pump bypass with limit switch	A-63

Control circuits with two actuators

Exercise 12:	Assembly device Pressure-dependent sequence control with cylinder and hydraulic motor	A-69
Exercise 13:	Lifting device for packages Position-dependent sequence control with two cylinders	A-75

We hope you enjoy the designing and practical assembly of the circuits.
Understanding hydraulics is fun!